

Problem Set 8 - Mitchell Kwock - Problem 3e

```
In [1]: import numpy as np
import matplotlib.pyplot as plt
%matplotlib inline
```

```
In [2]: def getRLC(w, r, l, c):
        '''
        Function returning the complex response of the system
        '''
        return 1.0/(1 + w * r * c * 1j - w * w * l * c)

def rlcHigh(r, l, c):
    '''
    Calculate location of the "Max". Derivation found on homework
    '''
    front = c / 2.0
    mid = 2 * l + 3 * r * r * c
    back = r * (6 * c * l + 9 * r * r * c * c)
    u = (front * (mid - back))
    omega = u ** -0.5
    return omega
```

```


In [3]: r = 400
        l = 1e-2
        c = 1e-7

        omegas = np.linspace(0, 100000, 1001)
        response = [np.abs(getRLC(w, r, l, c)) for w in omegas]
        high = rlcHigh(r, l, c)

        fig = plt.figure()
        ax = fig.add_subplot(1, 1, 1)
        ax.set_yscale('log')
        plt.plot(omegas, response)
        plt.plot([high, high], [1e-1, 1.2])
        plt.ylim([1e-1, 1.2])
        plt.title('Bode Plot for RLC Circuit where R=400\Omega, L=10^{-2}H, C=10^{-7}F')
        plt.xlabel('\omega')
        plt.ylabel('|H(\omega)| Logarithmic')

```

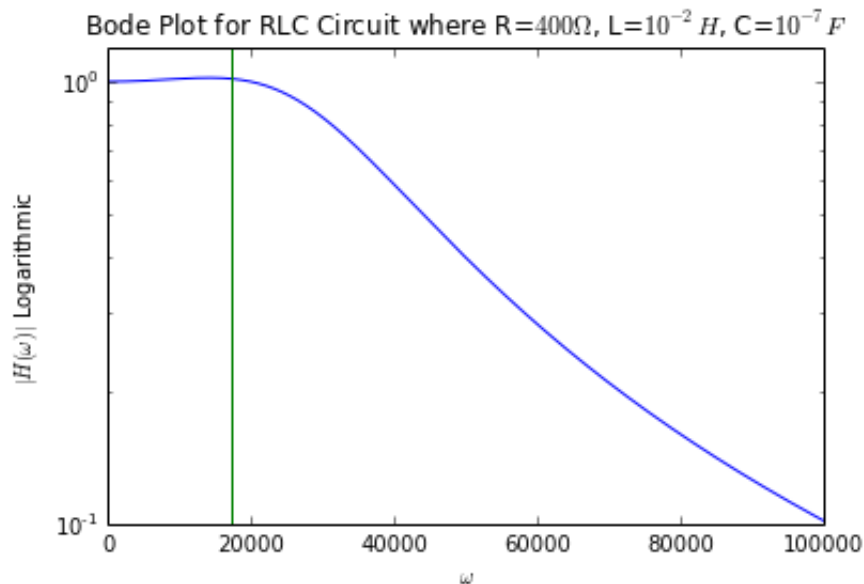Out[3]: <matplotlib.text.Text at 0xaa87c18>



```

In [4]: r = 50
        l = 1e-2
        c = 1e-7

        omegas = np.linspace(0, 100000, 1001)
        response = [np.abs(getRLC(w, r, l, c)) for w in omegas]
        high = rlcHigh(r, l, c)

        fig = plt.figure()
        ax = fig.add_subplot(1, 1, 1)
        ax.set_yscale('log')
        plt.plot(omegas, response)
        plt.plot([high, high], [1e-1, 10])
        plt.ylim([1e-1, 10])
        plt.title('Bode Plot for RLC Circuit where R=50\Omega, L=10^{-2}H, C=10^{-7}F')
        plt.xlabel('\omega')
        plt.ylabel('|H(\omega)| Logarithmic')

```

Out[4]: <matplotlib.text.Text at 0xb0b14e0>

